
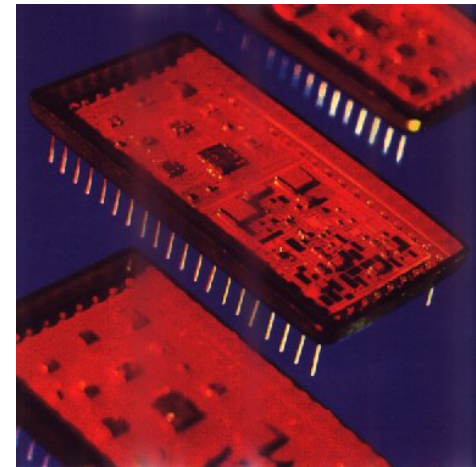


Contadores Especiais

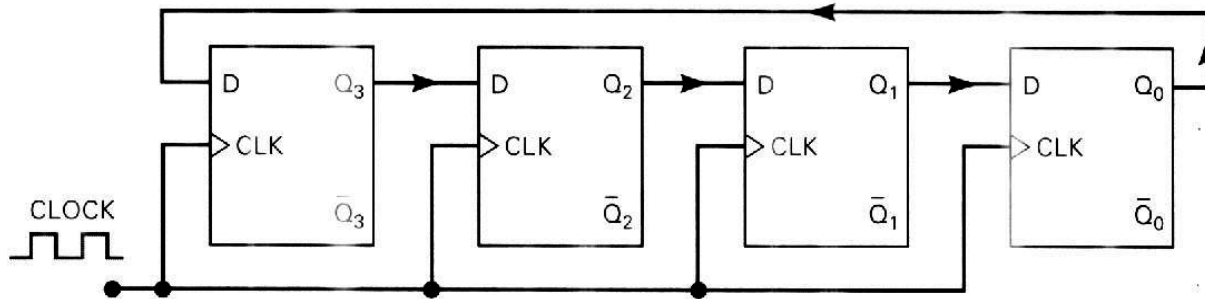
Circuitos Digitais II
Prof. Fernando Passold





(a)


Contador em Anel 4 bits

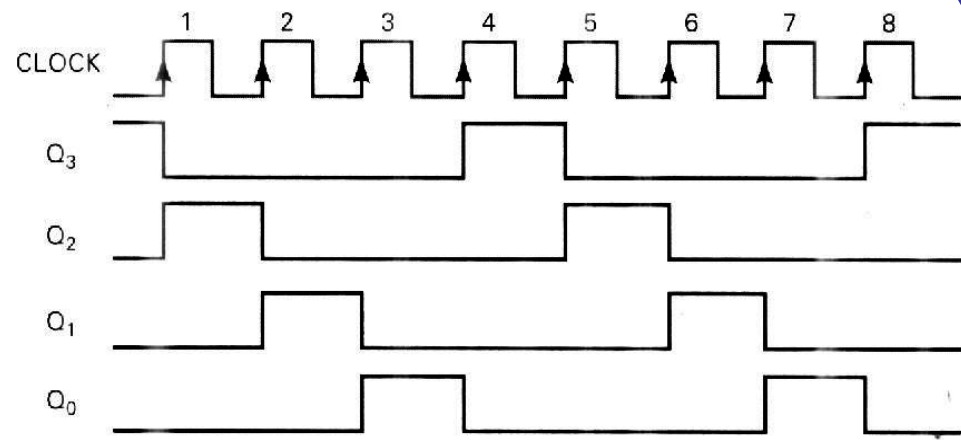

(b)


Q ₃	Q ₂	Q ₁	Q ₀	Pulso de CLOCK
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
·	·	·	·	·
·	·	·	·	·

(c)

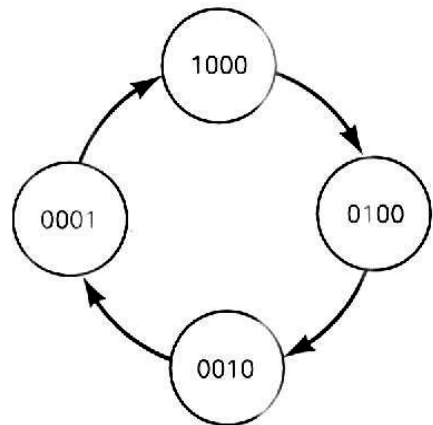


(d)

Figura:
 (a) Contador em anel de 4 bits;
 (b) Formas de onda;
 (c) Sequencia de contagem;
 (d) Diagrama de estados.

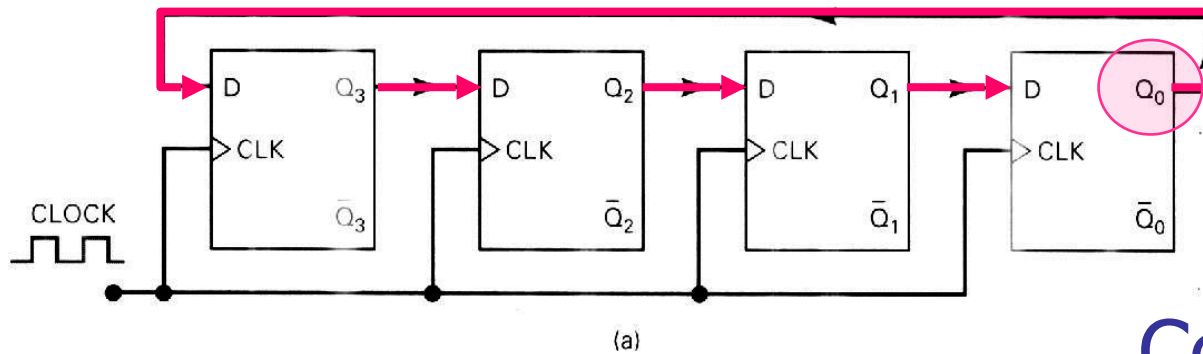


Contador em Anel 4 bits

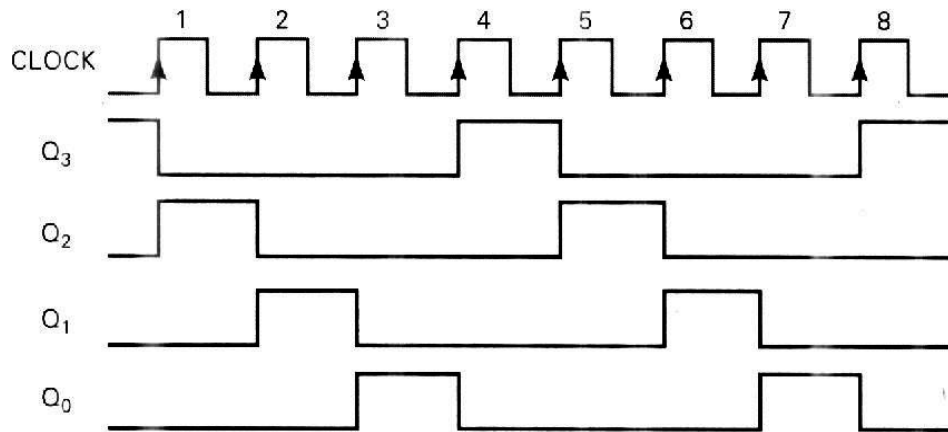

(b)

Q ₃	Q ₂	Q ₁	Q ₀	Pulso de CLOCK
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
·	·	·	·	·
·	·	·	·	·

(c)

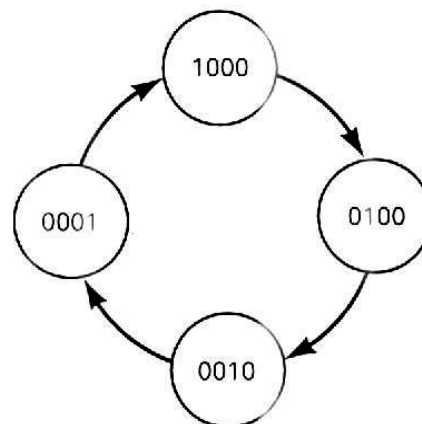


(d)


Fácil de obter: basta conectar as salidas dos FFs-D à entrada D do FF seguinte.

Figura:

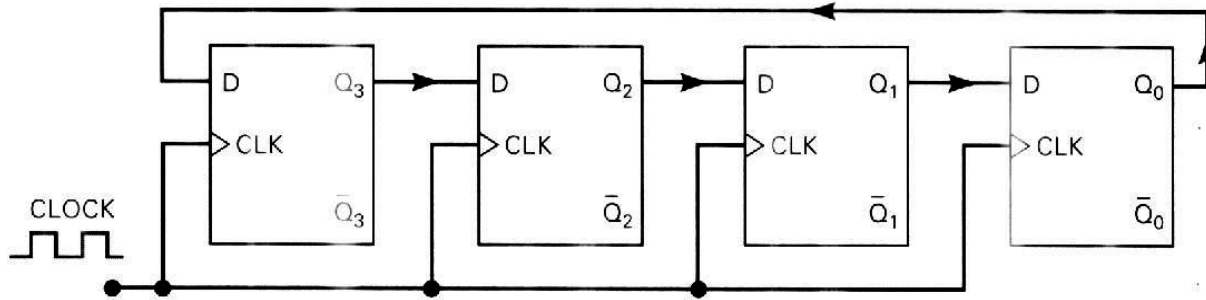- (a) Contador em anel de 4 bits;
- (b) Formas de onda;
- (c) Sequencia de contagem;
- (d) Diagrama de estados.




Contador em Anel 4 bits

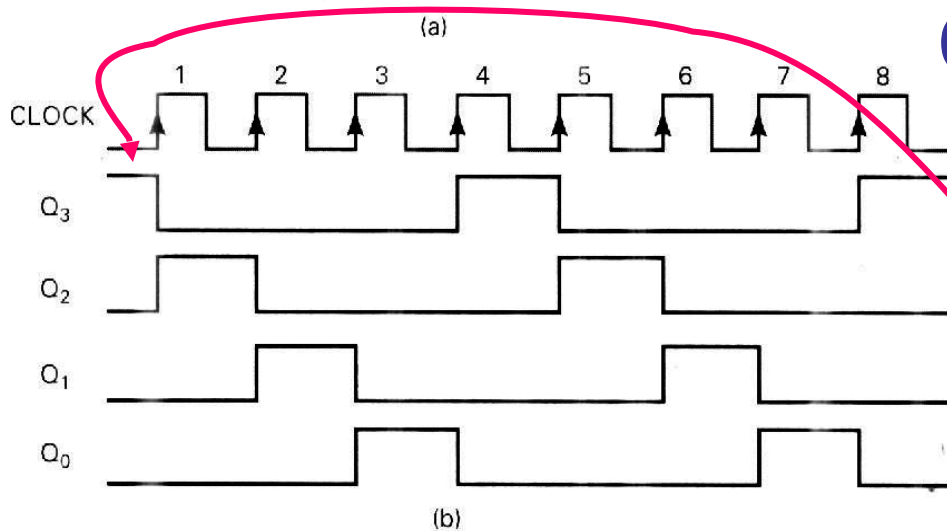


Q ₃	Q ₂	Q ₁	Q ₀	Pulso de CLOCK
1	0	0	0	0
0	1	0	0	1
0	0	1	0	2
0	0	0	1	3
1	0	0	0	4
0	1	0	0	5
0	0	1	0	6
0	0	0	1	7
⋮	⋮	⋮	⋮	⋮

(c)

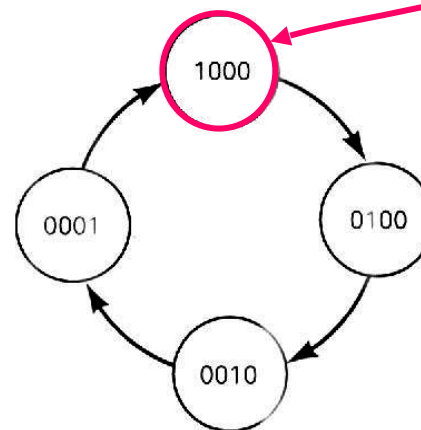



(d)

Problema: garantir este estado inicial

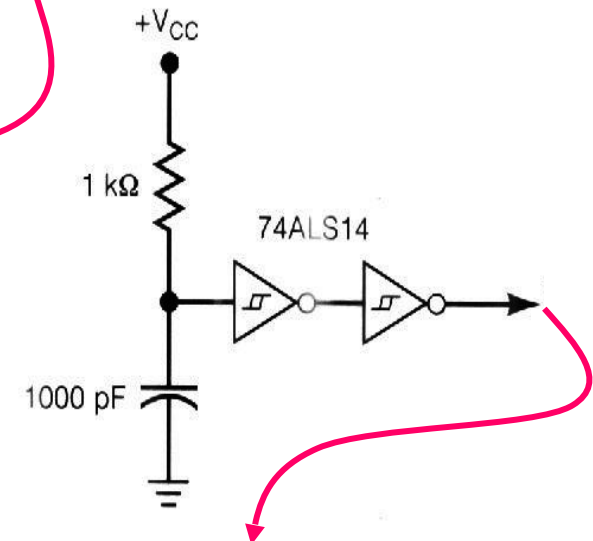


Para as entradas /PRE de Q₃ y /CLR de Q₂, Q₁ e Q₀ da figura (a).

Contador Johnson

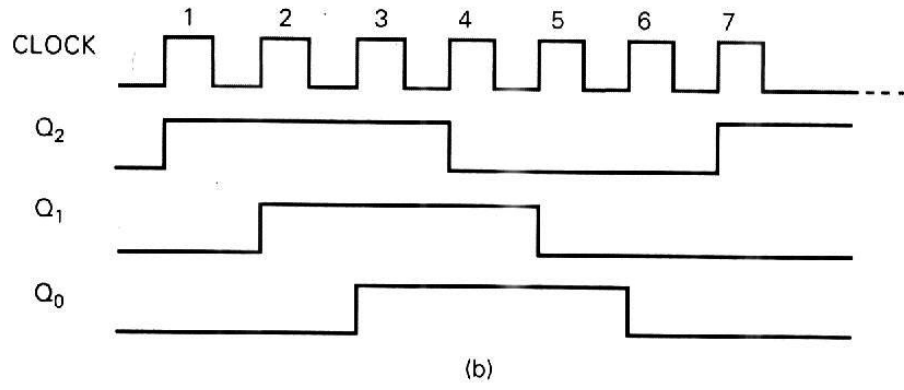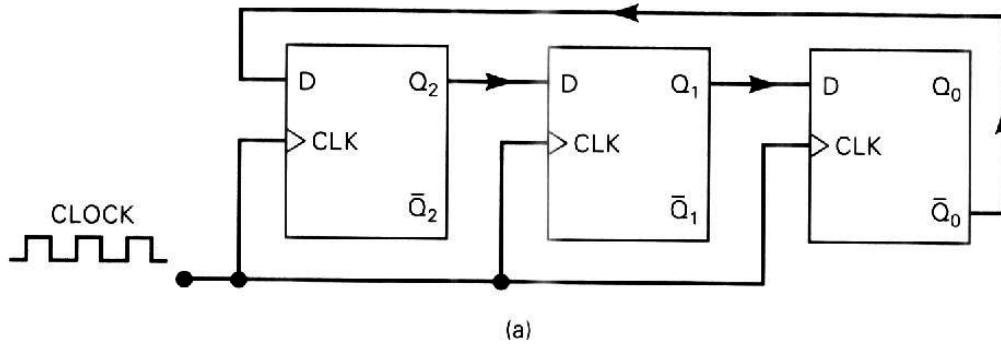


Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.

(c)

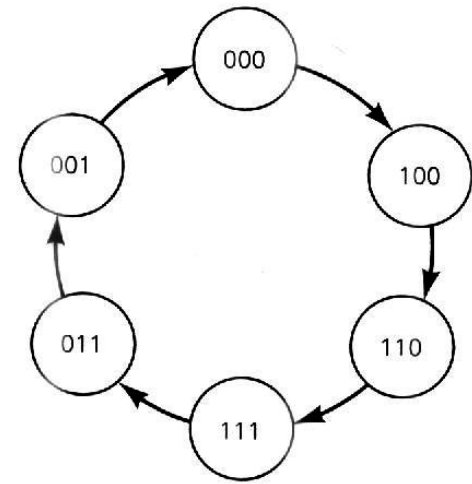


(d)

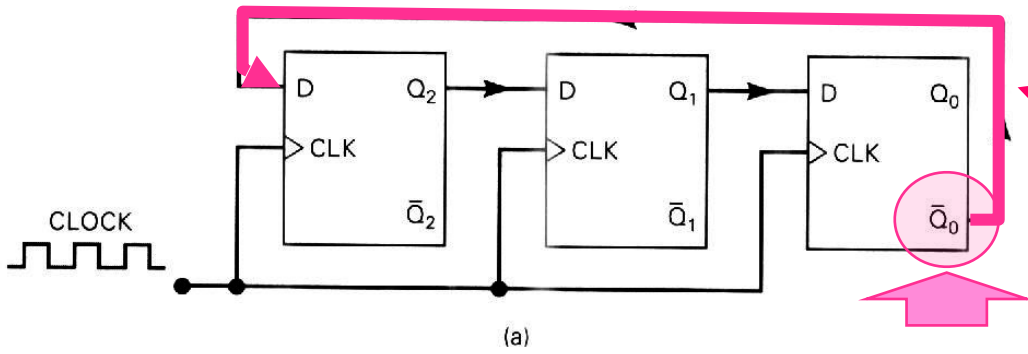

(a)

Contador Johnson

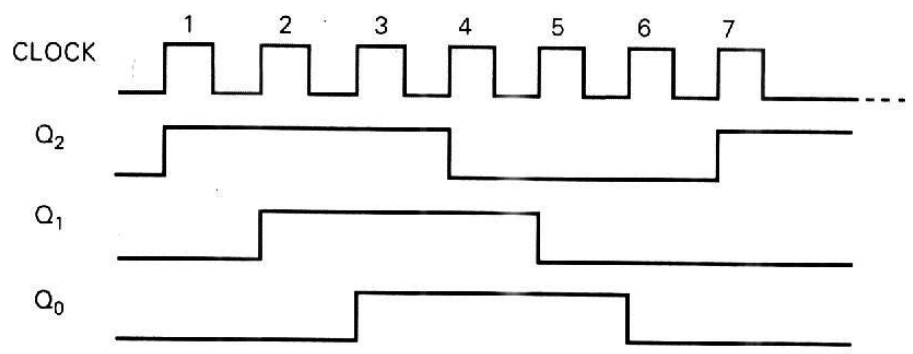


(b)

Fácil de obtener: basta conectar a entrada D do primeiro FF-D do contador ao complemento da saída do ultimo FF do contador.



Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.

(c)

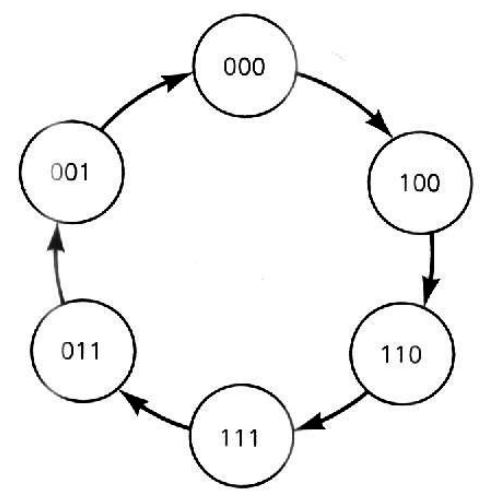


(d)

Aplicação ref. Contador Johnson:

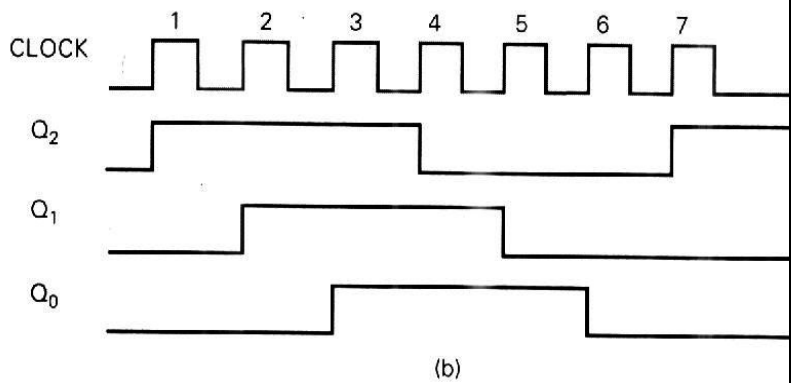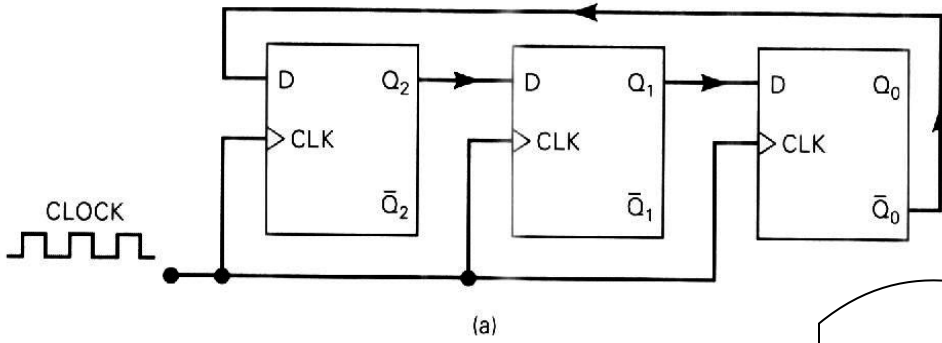

Contador com saídas decodificadas:

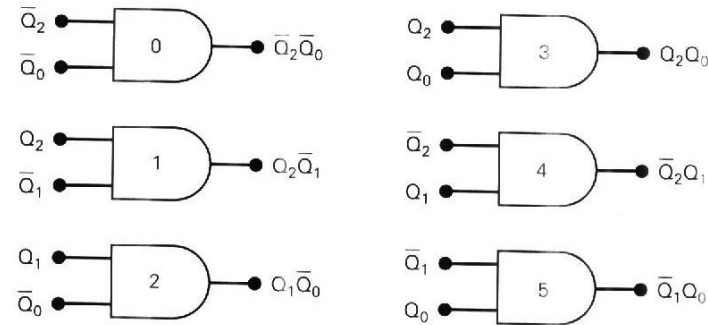

Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.


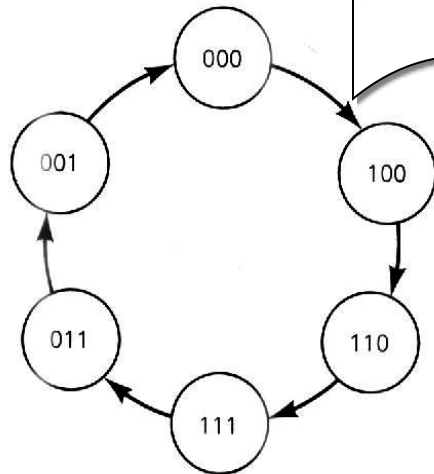


FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.


(c)

(d)

Aplicação ref. Contador Johnson:

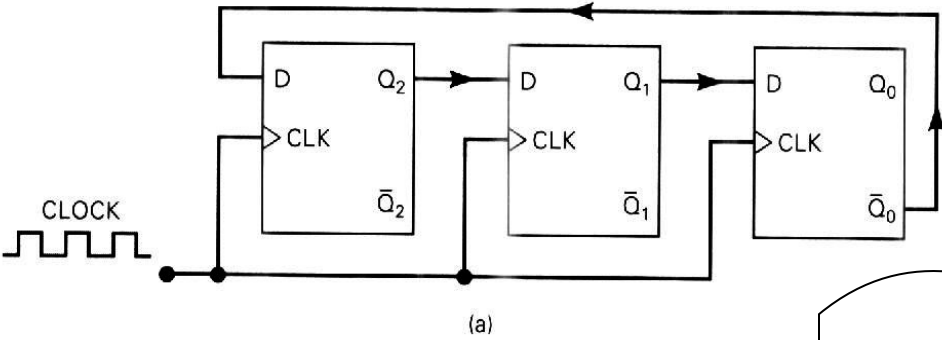


(a)

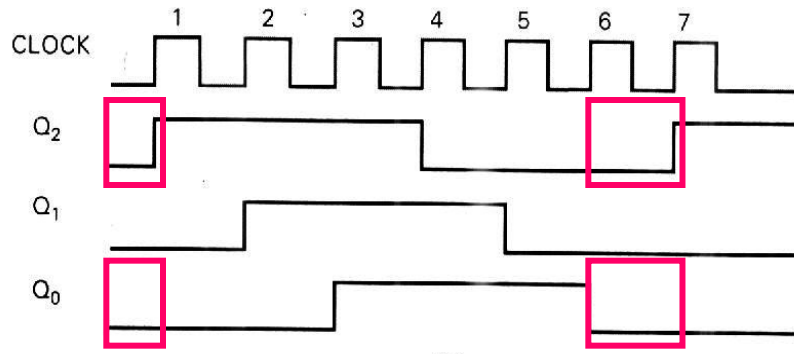

(b)

Contador com saídas decodificadas:

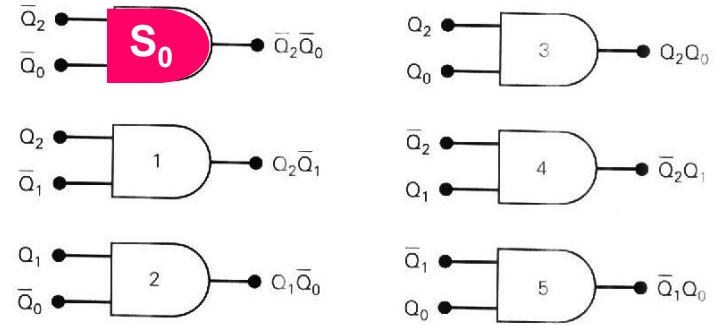


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.


Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.

(c)

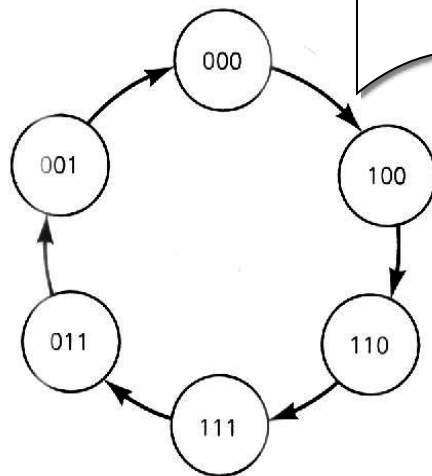


(d)

Aplicação ref. Contador Johnson:

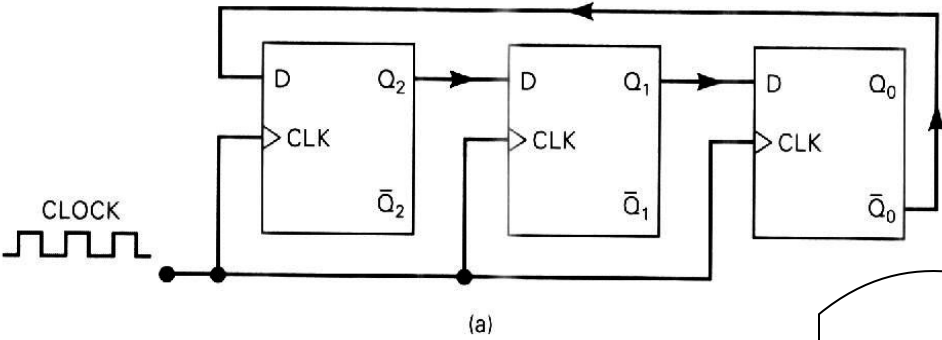


(a)

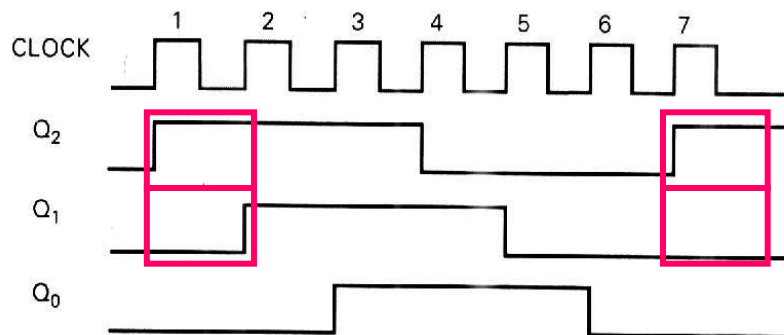

(b)

Contador com saídas decodificadas:

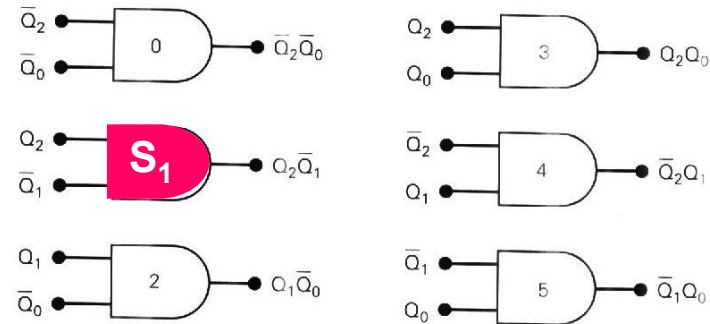


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.



Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.

(c)

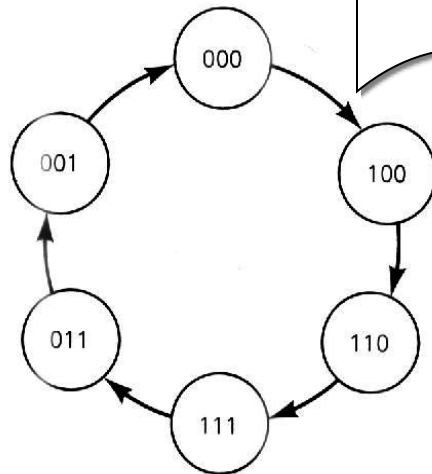

(d)


Aplicação ref. Contador Johnson:

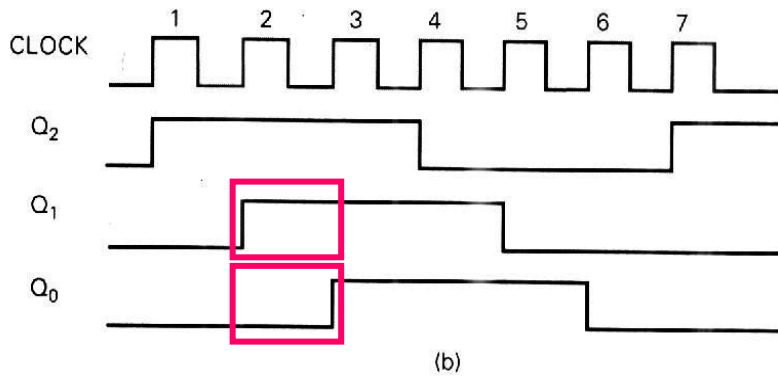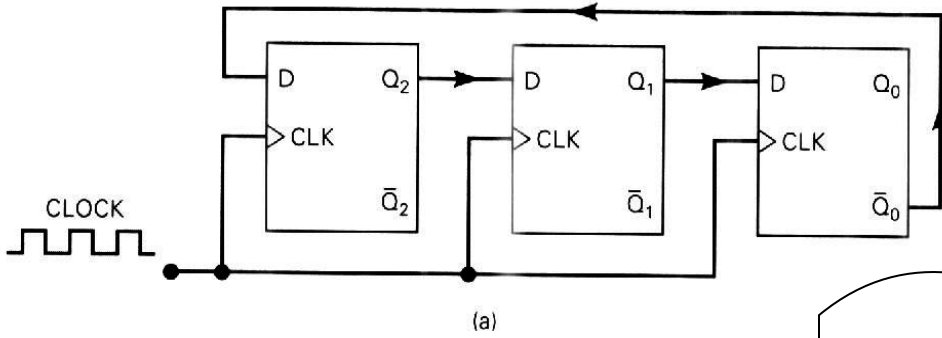

Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.


(c)

Contador com saídas decodificadas:

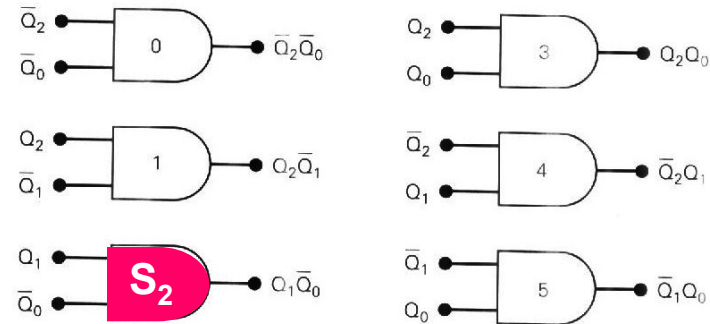



Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.

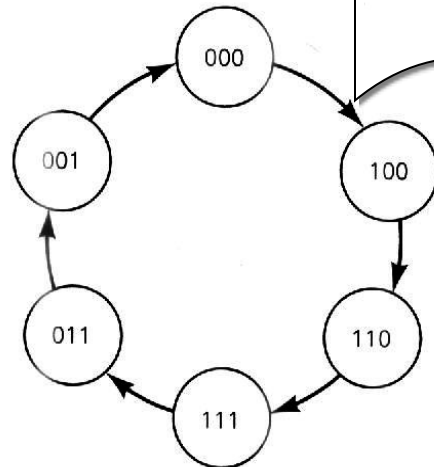


(d)

Aplicação ref. Contador Johnson:

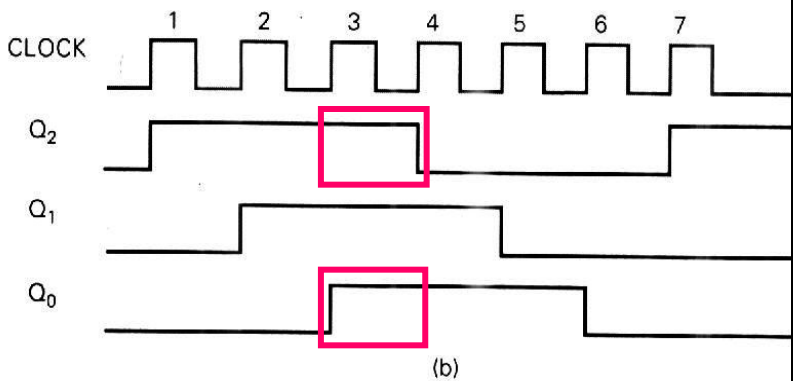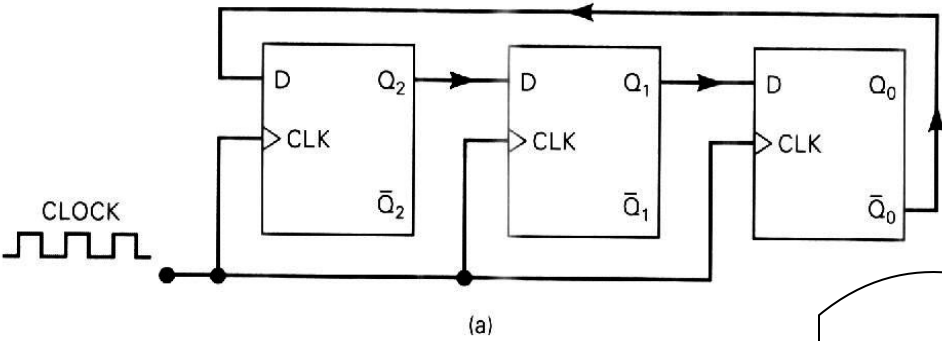


Contador com saídas decodificadas:

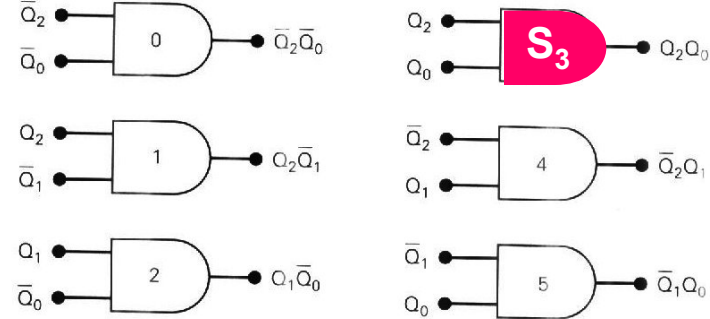


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.


Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
·	·	·	·
·	·	·	·

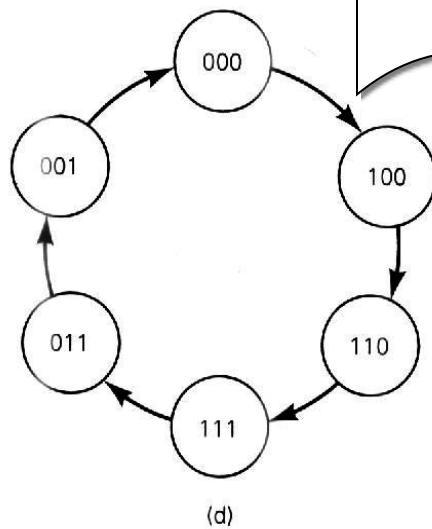

Aplicação ref. Contador Johnson:

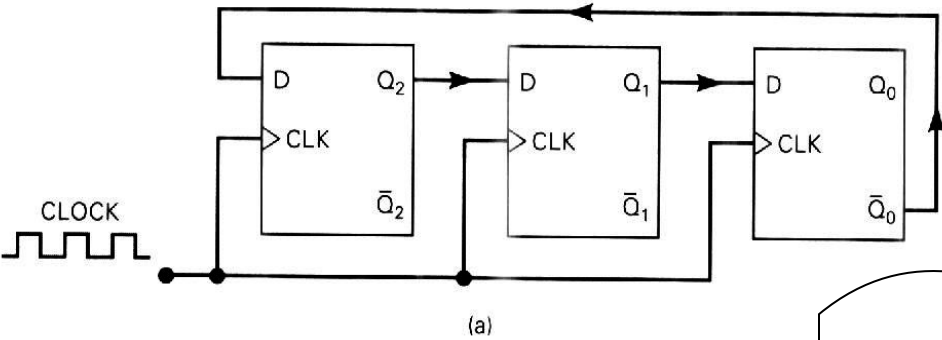


(a)

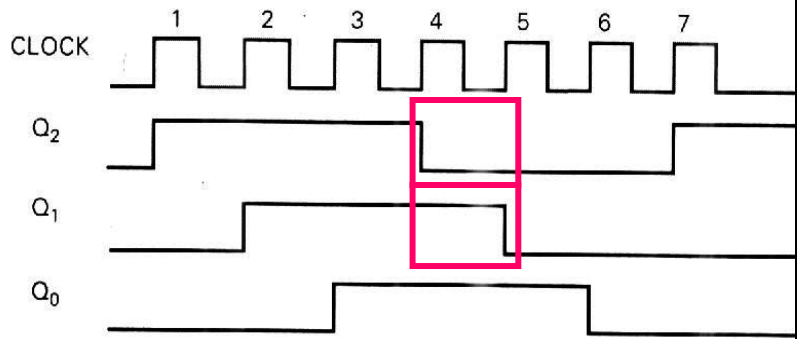

(b)

Contador com saídas decodificadas:

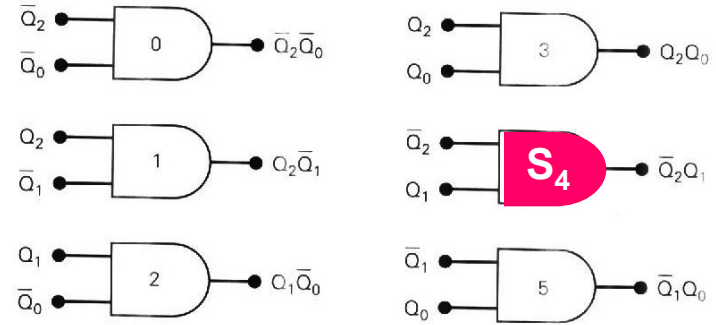


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.


Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.

(c)

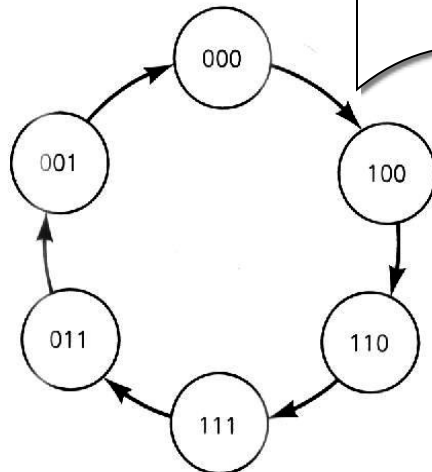


(d)

Aplicação ref. Contador Johnson:

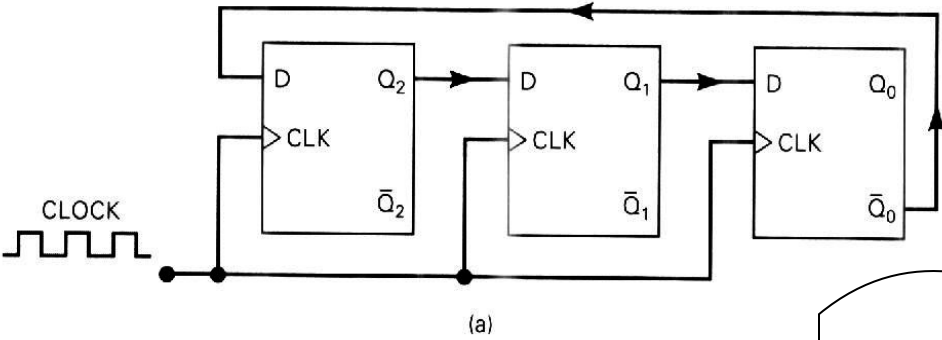


(a)

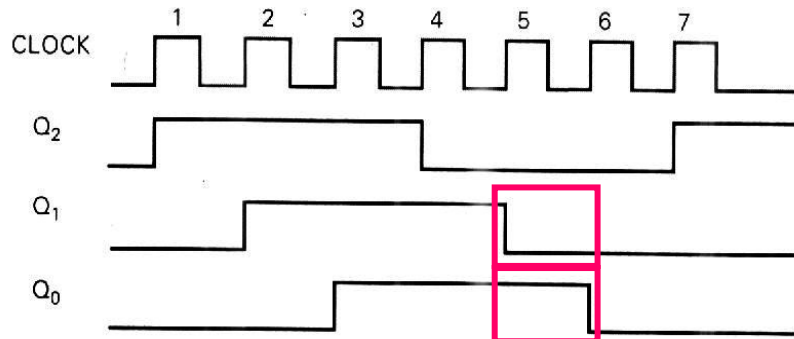

(b)

Contador com saídas decodificadas:

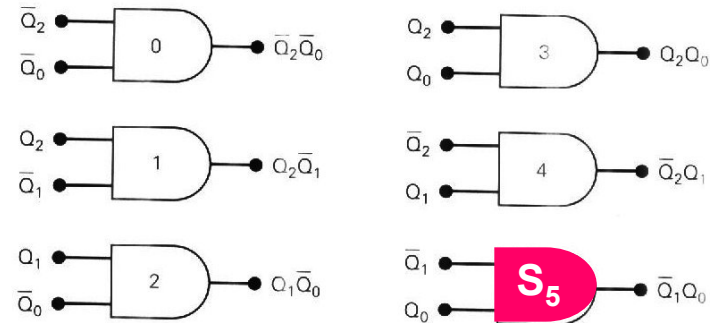


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.


Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.

(c)

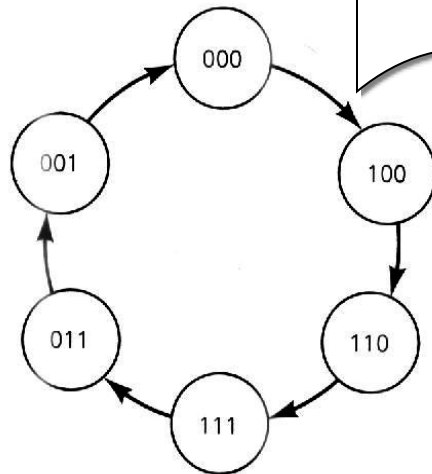


(d)

Aplicação ref. Contador Johnson:

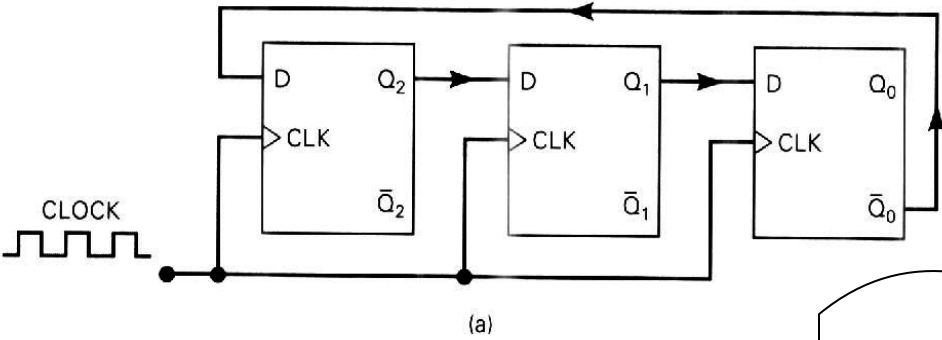


(a)

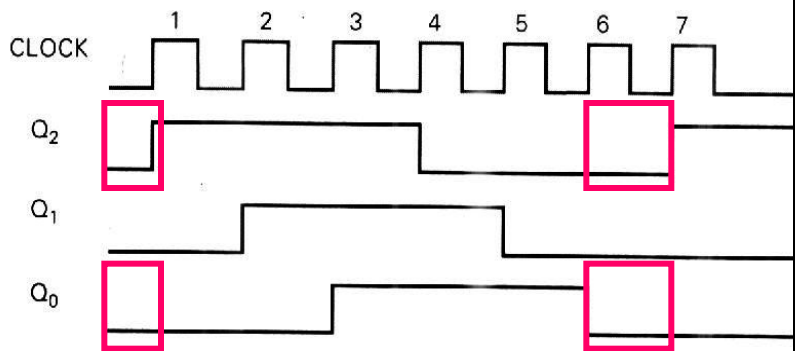

(b)

Contador com saídas decodificadas:

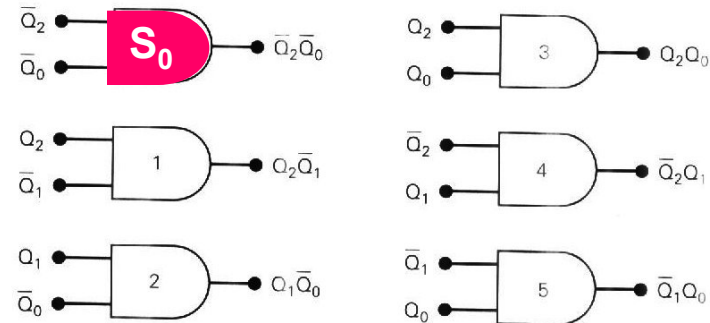


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.

Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.
.	.	.	.


(c)

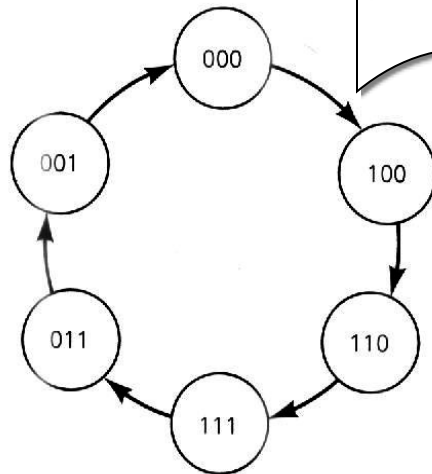


(d)

Notar que **no importa la cantidad de estados** del contador Johnson, siempre se puede decodificar sus salidas usando solamente puertas AND de 2 entradas!

Aplicação ref. Contador Johnson:

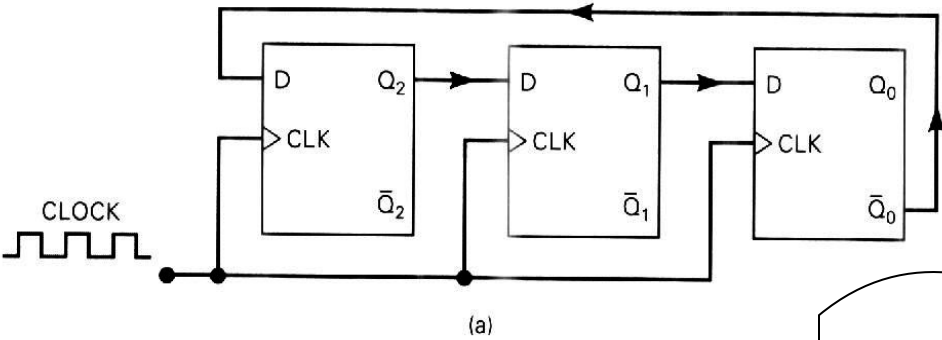


(a)

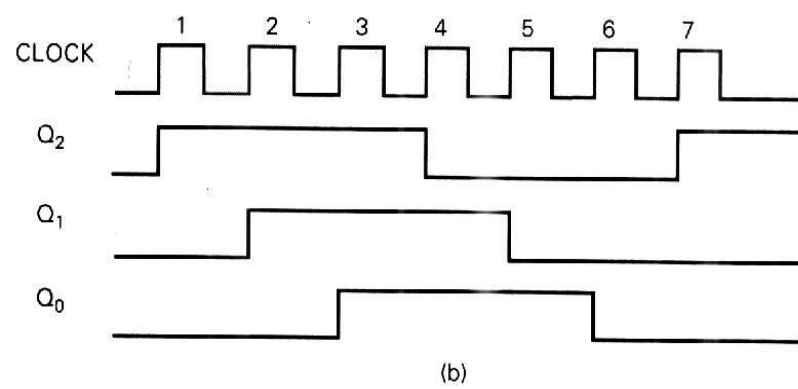

(b)


Contador com saídas decodificadas:

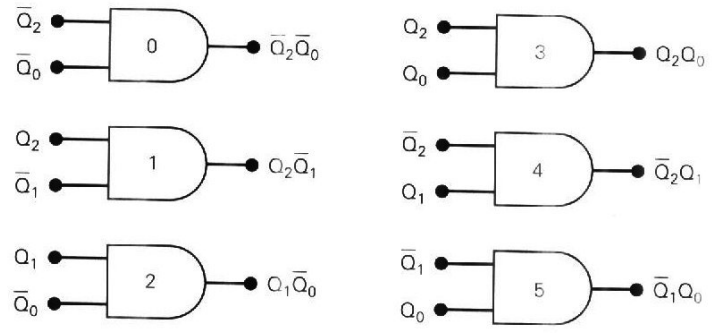

Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
.	.	.	.
.	.	.	.

(c)

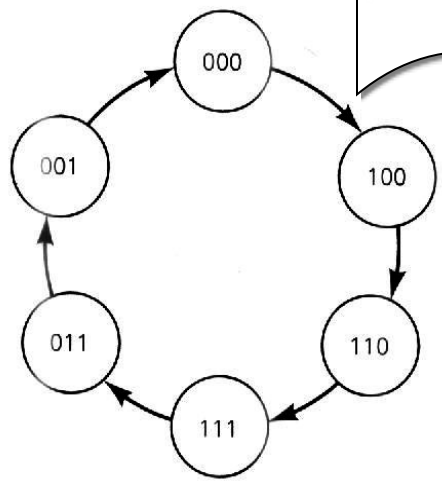


(d)


FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.

Vantagens:
 Não ocorrem os problemas de *glitches* comun aos contadores assíncronos com saídas decodificadas.

Aplicação ref. Contador Johnson:

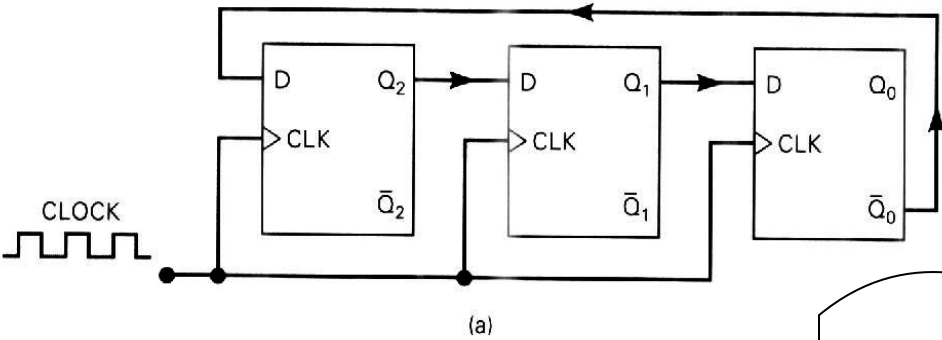


(a)

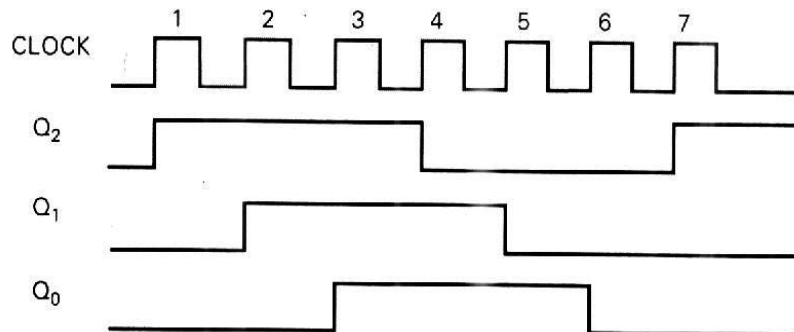

(b)

Contador com saídas decodificadas:

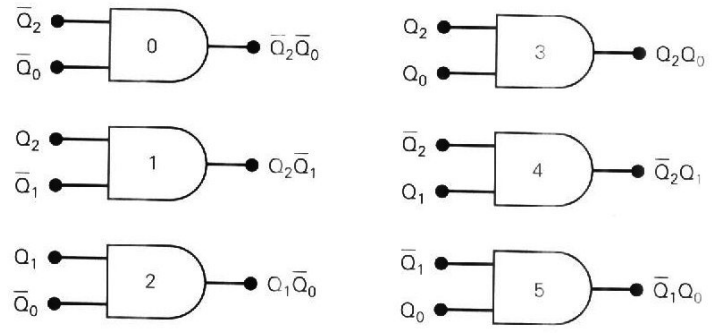


Q ₂	Q ₁	Q ₀	Porta ativa
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5

FIGURA 7.43 Lógica de decodificação para um contador Johnson de módulo 6.

Q ₂	Q ₁	Q ₀	Pulso de CLOCK
0	0	0	0
1	0	0	1
1	1	0	2
1	1	1	3
0	1	1	4
0	0	1	5
0	0	0	6
1	0	0	7
1	1	0	8
·	·	·	·
·	·	·	·

(c)

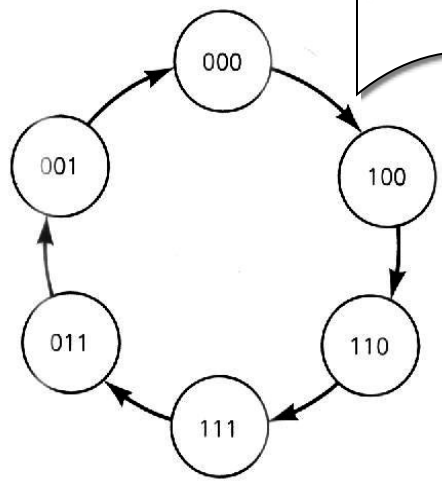

(d)

Notar também que **n estados** para un contador Johnson implica en **2×n FFs**.

CI de contador Johnson com saídas decodificadas:



October 1987

Revised January 1989

CD4017BC • CD4022BC

Decade Counter/Divider with 10 Decoded Outputs • Divide-by-8 Counter/Divider with 8 Decoded Outputs

General Description

The CD4017BC is a 5-stage divide-by-10 Johnson counter with 10 decoded outputs and a carry out bit.

The CD4022BC is a 4-stage divide-by-8 Johnson counter with 8 decoded outputs and a carry-out bit.

These counters are cleared to their zero count by a logical "1" on their reset line. These counters are advanced on the positive edge of the clock signal when the clock enable signal is in the logical "0" state.

The configuration of the CD4017BC and CD4022BC permits medium speed operation and assures a hazard free counting sequence. The 10/8 decoded outputs are normally in the logical "0" state and go to the logical "1" state only at their respective time slot. Each decoded output remains high for 1 full clock cycle. The carry-out signal completes a full cycle for every 10/8 clock input cycles and is used as a ripple carry signal to any succeeding stages.

Features

- Wide supply voltage range: 3.0V to 15V
- High noise immunity: 0.45 V_{DD} (typ.)
- Low power Fan out of 2 driving 74L
TTL compatibility: or 1 driving 74LS
- Medium speed operation: 5.0 MHz (typ.)
with 10V V_{DD}
- Low power: 10 μ W (typ.)
- Fully static operation

Applications

- Automotive
- Instrumentation
- Medical electronics
- Alarm systems
- Industrial electronics
- Remote metering

CD4017BC • CD4022BC
**Decade Counter/Divider with 10 Decoded Outputs •
 Divide-by-8 Counter/Divider with 8 Decoded Outputs**

 CI de contador
 Johnson com
 saídas
 decodificadas:

General Description

The **CD4017BC** is a 5-stage divide-by-10 Johnson counter with 10 decoded outputs and a carry out bit.


The CD4022BC is a 4-stage divide-by-8 Johnson counter with 8 decoded outputs and a carry-out bit.

These counters are cleared to their zero count by a logical "1" on their reset line. These counters are advanced on the positive edge of the clock signal when the clock enable signal is in the logical "0" state.

The configuration of the CD4017BC and CD4022BC permits medium speed operation and assures a hazard free counting sequence. The 10/8 decoded outputs are normally in the logical "0" state and go to the logical "1" state only at their respective time slot. Each decoded output remains high for 1 full clock cycle. The carry-out signal completes a full cycle for every 10/8 clock input cycles and is used as a ripple carry signal to any succeeding stages.

Timing Diagrams

CD 4017:

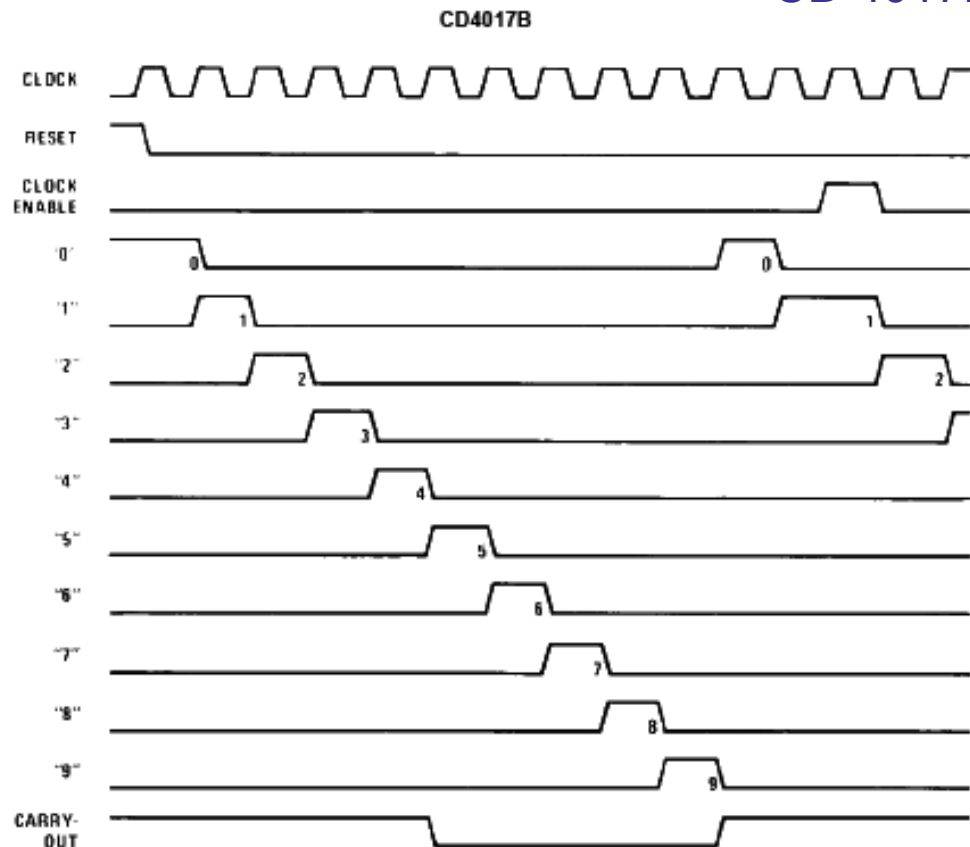

CD4017BC • CD4022BC

Decade Counter/Divider with 10 Decoded Outputs • Divide-by-8 Counter/Divider with 8 Decoded Outputs

CI de contador
 Johnson com
 saídas
 decodificadas:

General Description


The CD4017BC is a 5-stage divide-by-10 Johnson counter with 10 decoded outputs and a carry out bit.

The CD4022BC is a 4-stage divide-by-8 Johnson counter with 8 decoded outputs and a carry-out bit.

These counters are cleared to their zero count by a logical "1" on their reset line. These counters are advanced on the positive edge of the clock signal when the clock enable signal is in the logical "0" state.

The configuration of the CD4017BC and CD4022BC permits medium speed operation and assures a hazard free counting sequence. The 10/8 decoded outputs are normally in the logical "0" state and go to the logical "1" state only at their respective time slot. Each decoded output remains high for 1 full clock cycle. The carry-out signal completes a full cycle for every 10/8 clock input cycles and is used as a ripple carry signal to any succeeding stages.

CD 4022:

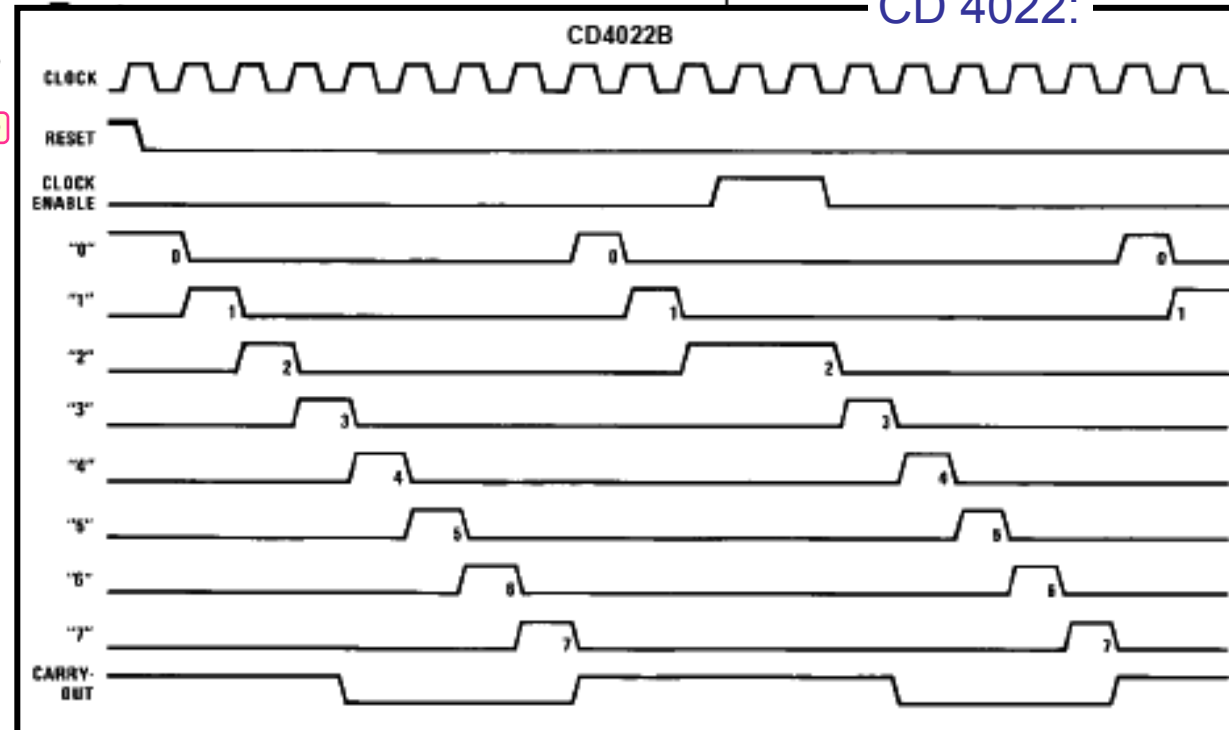

Contador (síncrono) com carga paralela de dados:

